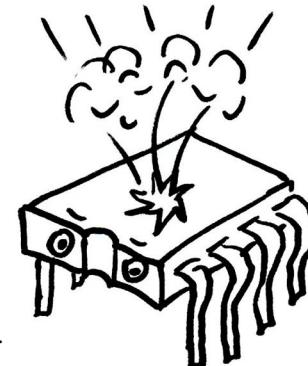


TR-808 bass drum project

handwired perfboard construction

<http://ericarcher.net/devices/tr808-clone/>

Eric Archer 2009



This analog bass drum circuit is adapted from the schematic in the TR-808 Service Manual. Transistors have been substituted. It is intended to be close to the original sound.

I built it on PC-4 perfboard. you could use any pad-per-hole 0.1" grid board though. Dont build this on a solderless breadboard - you wont want to take it apart!

The layout doesnt include a power connector. The circuit needs +/-15V or +/-12V. You'll have to add the power connections.

Look carefully at the PWR page. The positive and negative supply rails are shown but not labeled as to which is which.

Remember that pin 8 of the TL072 is (+) and pin 4 is (-)... then you'll see which is which.

And you'll have to add an ouput jack of some sort. for output I just wired up a 3.5mm mono plug run it into a mixer.

If you are planning on triggering the circuit from a logic signal, the easiest way is to tie ACCENT to +12V (+15V), and connect the logic signal to TRIGGER. This schematic includes my diode-cap-resistor network. This makes trigger behavior independent of pulse width (unless the pulse is super short of course)

I laid this circuit out with larger footprint film caps.

---- construction procedure ---


start by printing out the four pages with wiring routing on them.

STEP 1: referring to the **placement** and **values** pages, install all the components on the perfboard.

STEP 2: referring to **GND**, **PWR**, **routing1**, and **routing2**, make all the connections that are possible by bending and cutting component leads. use fine tipped needle nose pliers to bend the leads so they make efficient connections. make sure you thoroughly heat all solder joints so there arent any surprise open circuits later.

on the printouts, carefully trace all connections as you make them, using a colored pen or highlighter. that way you can keep track of whats left to do; when all the lines are traced, the wiring is done.

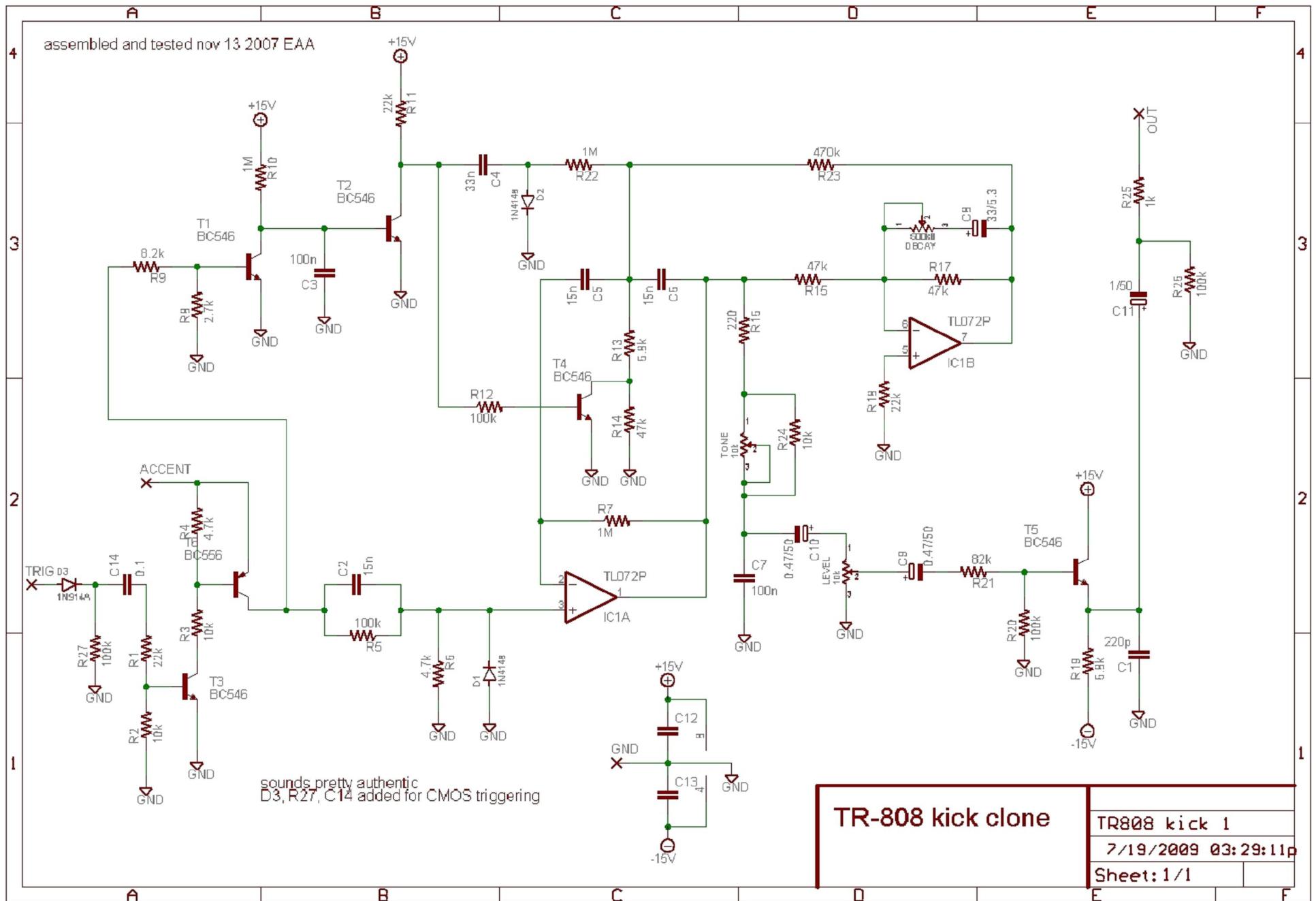STEP 3: finish the remaining connections using short pieces of wire. 30- or 28- gauge "wire wrap" wire is recommended. this is solid core wire with high-temperature insulation. to do the wiring reliably, you really need high temperature insulation that doesn't shrink when heated. Strip the wires carefully so you don't nick the conductor and make an unreliable connection.



TR-808 KICK DRUM

NOV 13 2007 EAA

741

741

741

ACC TRIG GND


2225

1 2 3 4 5 6 7 8 9 10 11 12 13 14 15 16 17 18 19 20 21 22 23 24 25 26 27 28 29 30 31 32 33 34 35 36

Layout by EAA

LEVEL
TONE
DECAY

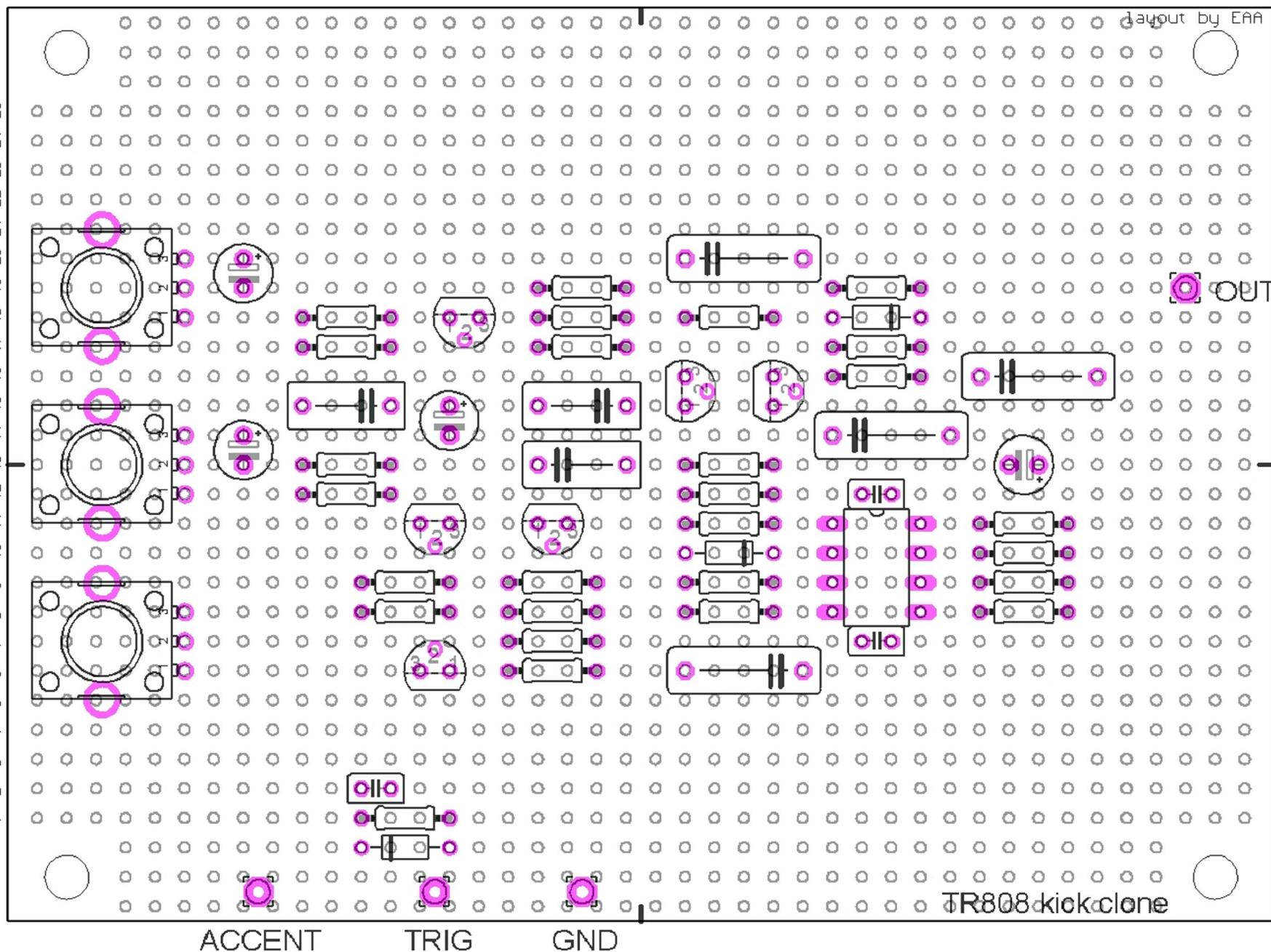1 2 3 4 5 6 7 8 9 10 11 12 13 14 15 16 17 18 19 20 21 22 23 24 25




placement

1 2 3 4 5 6 7 8 9 10 11 12 13 14 15 16 17 18 19 20 21 22 23 24 25

layout by EAA

LEVEL
TONE
DECAY

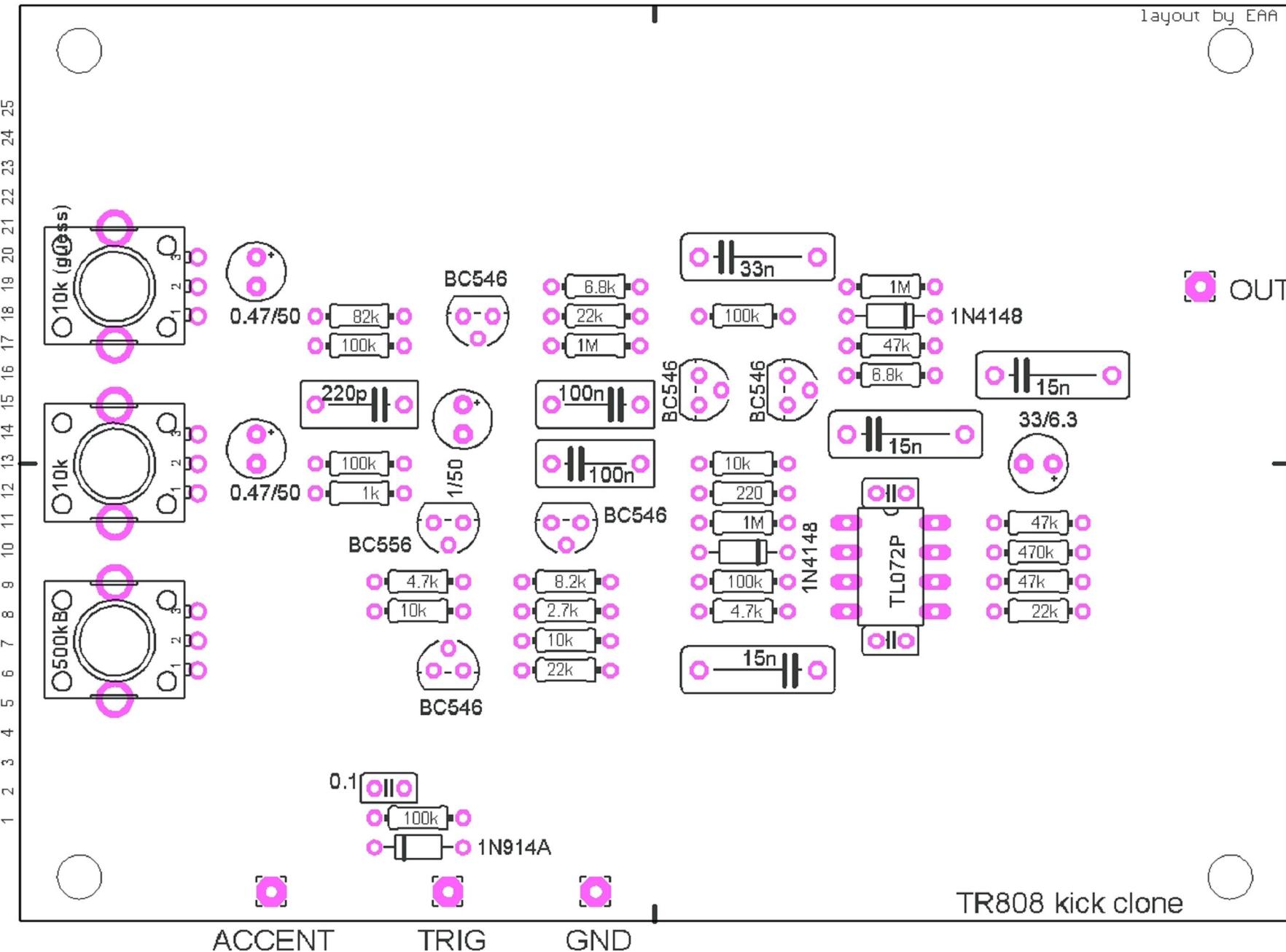


1 2 3 4 5 6 7 8 9 10 11 12 13 14 15 16 17 18 19 20 21 22 23 24 25 26 27 28 29 30 31 32 33 34 35 36


layout by EAA

LEVEL
TONE
DECAY

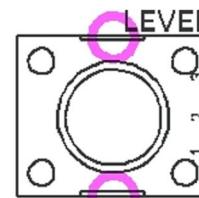
1 2 3 4 5 6 7 8 9 10 11 12 13 14 15 16 17 18 19 20 21 22 23 24 25



C9

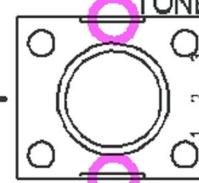

C10

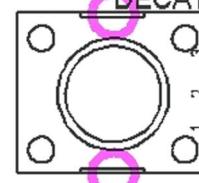

C11

C14

ACCENT

R27

D3 TRIG

R26

R25

R4

R3

R9

R8

R2

R1

T1

T6

T3

T5

T2

C1

C3

C7

C4

R19

R11

R10

R12

R14

R13

C5

R24

R18

R7

D1

R5

R6

C2

IC1

C12

C13

GND


TR808 kick clone

names

1 2 3 4 5 6 7 8 9 10 11 12 13 14 15 16 17 18 19 20 21 22 23 24 25

layout by EAA

LEVEL
TONE
DECAY

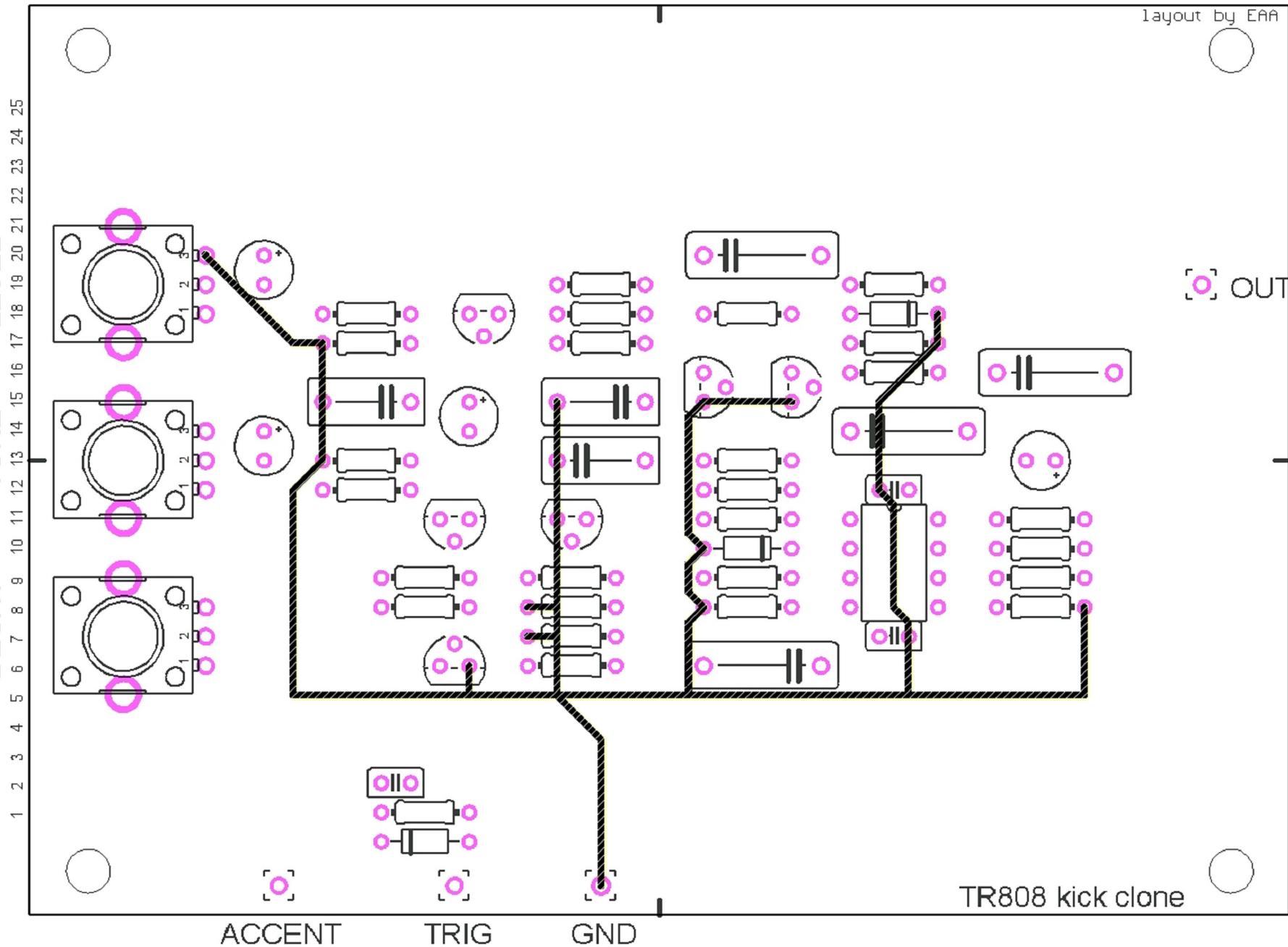


TR808 kick clone

GND

1 2 3 4 5 6 7 8 9 10 11 12 13 14 15 16 17 18 19 20 21 22 23 24 25 26 27 28 29 30 31 32 33 34 35 36

layout by EAA

LEVEL
TONE
DECAY

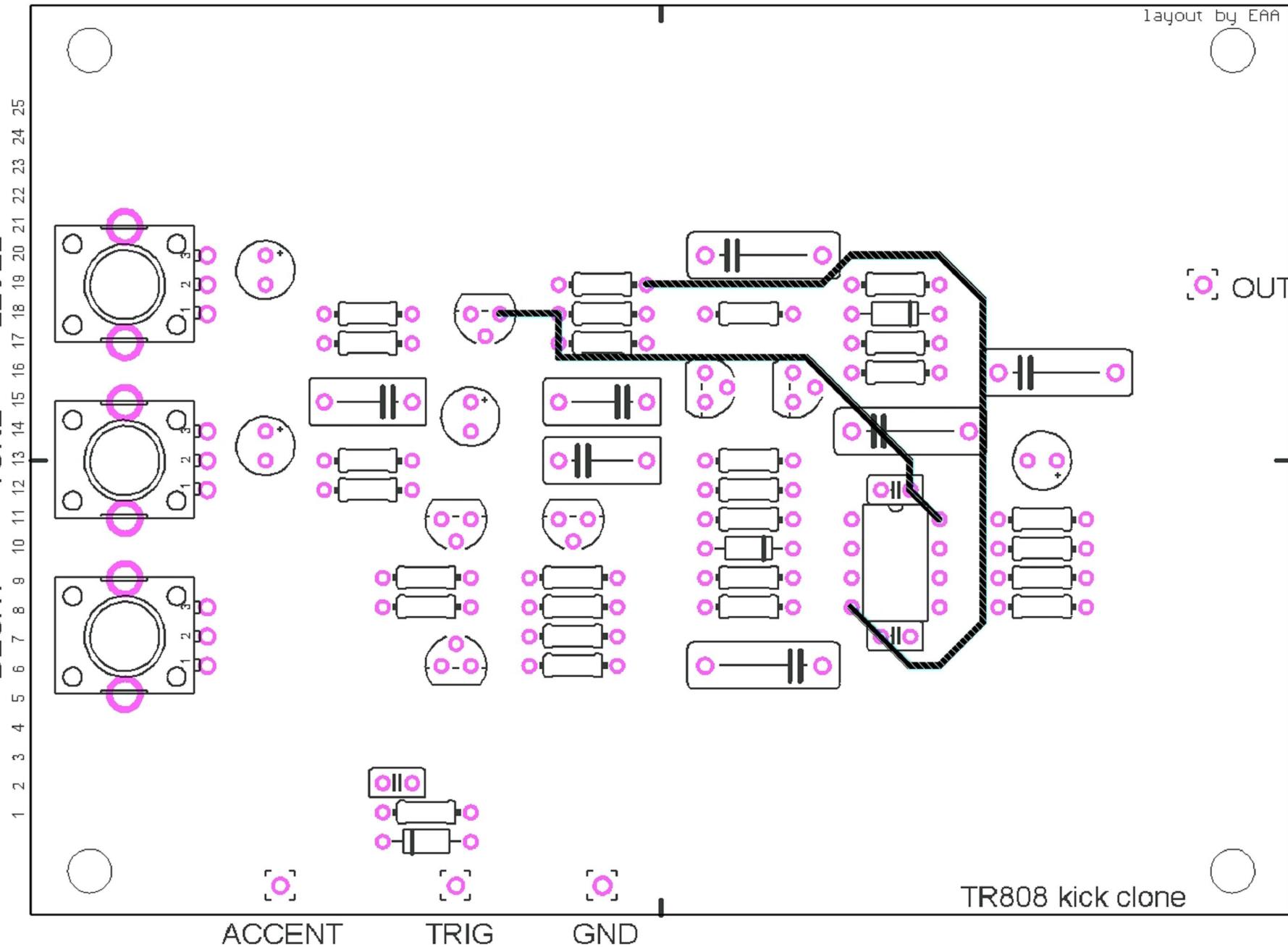

TR808 kick clone

PWR

1 2 3 4 5 6 7 8 9 10 11 12 13 14 15 16 17 18 19 20 21 22 23 24 25

layout by EAA


25 24 23 22 21 20 19 18 17 16 15 14 13 12 11 10 9 8 7 6 5 4 3 2 1

LEVEL
16 17 18 19 20 21 22 23 24 25

TONE
11 12 13 14 15 16 17 18 19 20 21 22 23 24 25

DECAY
10 11 12 13 14 15 16 17 18 19 20 21 22 23 24 25

9 8 7 6 5 4 3 2 1

 

ACCENT

TRIG

GND

TR808 kick clone

route1

1 2 3 4 5 6 7 8 9 10 11 12 13 14 15 16 17 18 19 20 21 22 23 24 25

layout by EAA

25 24 23 22 21 20 19 18 17 16 15 14 13 12 11 10 9 8 7 6 5 4 3 2 1

LEVEL
TONE
DECAY

25 24 23 22 21 20 19 18 17 16 15 14 13 12 11 10 9 8 7 6 5 4 3 2 1

25 24 23 22 21 20 19 18 17 16 15 14 13 12 11 10 9 8 7 6 5 4 3 2 1

25 24 23 22 21 20 19 18 17 16 15 14 13 12 11 10 9 8 7 6 5 4 3 2 1

25 24 23 22 21 20 19 18 17 16 15 14 13 12 11 10 9 8 7 6 5 4 3 2 1

25 24 23 22 21 20 19 18 17 16 15 14 13 12 11 10 9 8 7 6 5 4 3 2 1

25 24 23 22 21 20 19 18 17 16 15 14 13 12 11 10 9 8 7 6 5 4 3 2 1

25 24 23 22 21 20 19 18 17 16 15 14 13 12 11 10 9 8 7 6 5 4 3 2 1

25 24 23 22 21 20 19 18 17 16 15 14 13 12 11 10 9 8 7 6 5 4 3 2 1

25 24 23 22 21 20 19 18 17 16 15 14 13 12 11 10 9 8 7 6 5 4 3 2 1

25 24 23 22 21 20 19 18 17 16 15 14 13 12 11 10 9 8 7 6 5 4 3 2 1

25 24 23 22 21 20 19 18 17 16 15 14 13 12 11 10 9 8 7 6 5 4 3 2 1

25 24 23 22 21 20 19 18 17 16 15 14 13 12 11 10 9 8 7 6 5 4 3 2 1

25 24 23 22 21 20 19 18 17 16 15 14 13 12 11 10 9 8 7 6 5 4 3 2 1

25 24 23 22 21 20 19 18 17 16 15 14 13 12 11 10 9 8 7 6 5 4 3 2 1

25 24 23 22 21 20 19 18 17 16 15 14 13 12 11 10 9 8 7 6 5 4 3 2 1

25 24 23 22 21 20 19 18 17 16 15 14 13 12 11 10 9 8 7 6 5 4 3 2 1

25 24 23 22 21 20 19 18 17 16 15 14 13 12 11 10 9 8 7 6 5 4 3 2 1

25 24 23 22 21 20 19 18 17 16 15 14 13 12 11 10 9 8 7 6 5 4 3 2 1

25 24 23 22 21 20 19 18 17 16 15 14 13 12 11 10 9 8 7 6 5 4 3 2 1

25 24 23 22 21 20 19 18 17 16 15 14 13 12 11 10 9 8 7 6 5 4 3 2 1

25 24 23 22 21 20 19 18 17 16 15 14 13 12 11 10 9 8 7 6 5 4 3 2 1

25 24 23 22 21 20 19 18 17 16 15 14 13 12 11 10 9 8 7 6 5 4 3 2 1

25 24 23 22 21 20 19 18 17 16 15 14 13 12 11 10 9 8 7 6 5 4 3 2 1

OUT

TR808 kick clone

route2

ACCENT

TRIG

GND

Transistors:
 5x 2SC945 (P) NPN
 1x 2SA733 (P) PNP

2x 1n4148 Diode
 1x TL072 Dual OP-AMP

Electrolytic Cap:
 2x 0,47 μ F/50V
 1x 1 μ F/50V
 1x 33 μ F/6,3V
 2x 47 μ F/16V (PWR bypass)


Caps:
 1x 220p
 3x 15n
 1x 33n
 2x 100n

Potentiometers:
 1x 500k Lin
 1x 10K Log
 1x 100K Lin

Resistors 1/4W 1%:

C61 .0068 to .015
 R191 8.2k to 10k
 R200 47k to zero

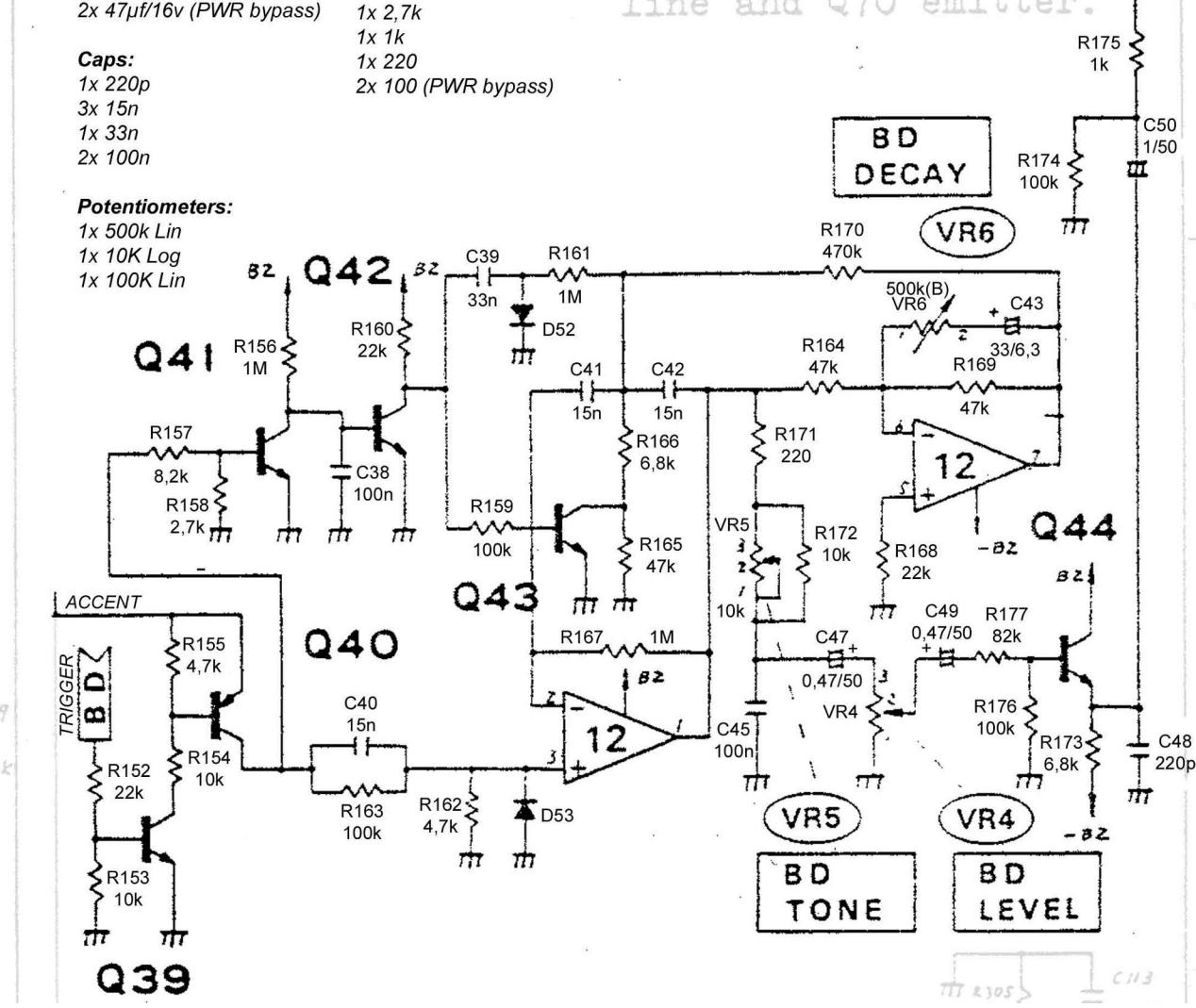C P
 10k (called R200) is
 connected across -15V
 line and Q70 emitter.



original